

# Gate Question

## SECTION A

February 2, 2024

1. In the circuit shown below, assume that the comparators are ideal and all components have zero propagation delay. In one period of the input signal  $V_{in} = 6 \sin(\omega t)$ , the fraction of the time for which the output OUT is in logic HIGH is (GATE-IN2019,34)

 


Figure 1: Circuit Daigram

1.  $\frac{1}{12}$
2.  $\frac{1}{2}$
3.  $\frac{2}{3}$
4.  $\frac{5}{6}$